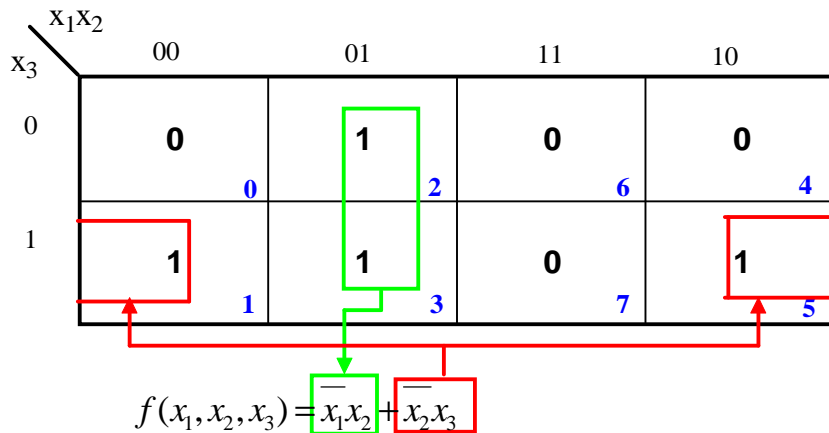


4.1 Find the minimum-cost SOP and POS forms for the function  $f(x_1, x_2, x_3) = \sum m(1, 2, 3, 5)$ .

Solution:


$$f(x_1, x_2, x_3) = \sum m(1, 2, 3, 5)$$



Mapping the 1's from the K-map as follows

$f(x_1, x_2, x_3) = \overline{x_1}x_2 + x_2x_3$  - This is the minimum-cost SOP form.
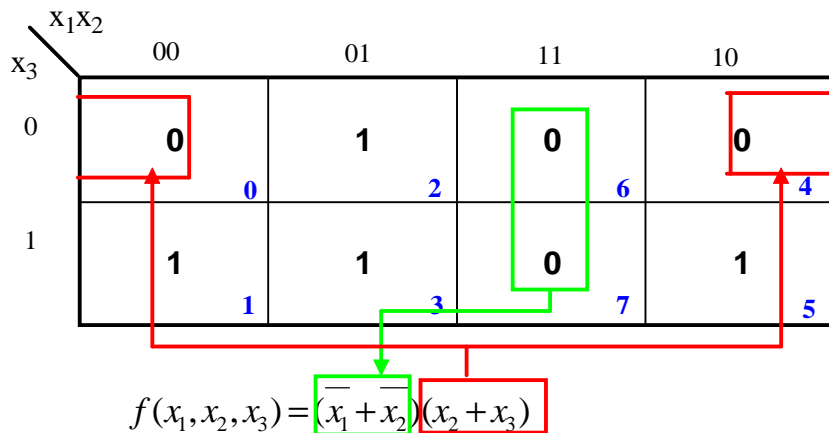
$$f(x_1, x_2, x_3) = \sum m(1, 2, 3, 5)$$



Mapping the 0's from the K-map as follows

$f(x_1, x_2, x_3) = (\overline{x_1} + \overline{x_2})(x_2 + x_3)$  - This is the minimum-cost POS form.

4.2 Repeat problem 4.1 for the function  $f(x_1, x_2, x_3) = \sum m(1, 4, 7) + D(2, 5)$ .

Solution:

$$f(x_1, x_2, x_3) = \sum m(1,4,7) + D(2,5)$$

		$x_1x_2$			
		00	01	11	10
$x_3$	0	0	d	0	1
	1	1	0	1	d

$$f(x_1, x_2, x_3) = \overline{x_2}x_3 + x_1x_3 + x_1x_2$$

Mapping the 1's from the K-map as follows

$f(x_1, x_2, x_3) = \overline{x_2}x_3 + x_1x_3 + x_1x_2$  -This is the minimum-cost SOP form.

$$f(x_1, x_2, x_3) = \sum m(1,4,7) + D(2,5)$$

		$x_1x_2$			
		00	01	11	10
$x_3$	0	d	0	1	
	1	1	0	d	

$$f(x_1, x_2, x_3) = (x_1 + x_3)(x_1 + x_2)(\overline{x_2} + x_3)$$


Mapping the 0's from the K-map as follows

$f(x_1, x_2, x_3) = (\overline{x_2} + x_3)(x_1 + x_3)(x_1 + \overline{x_2})$  This is the minimum-cost POS form.

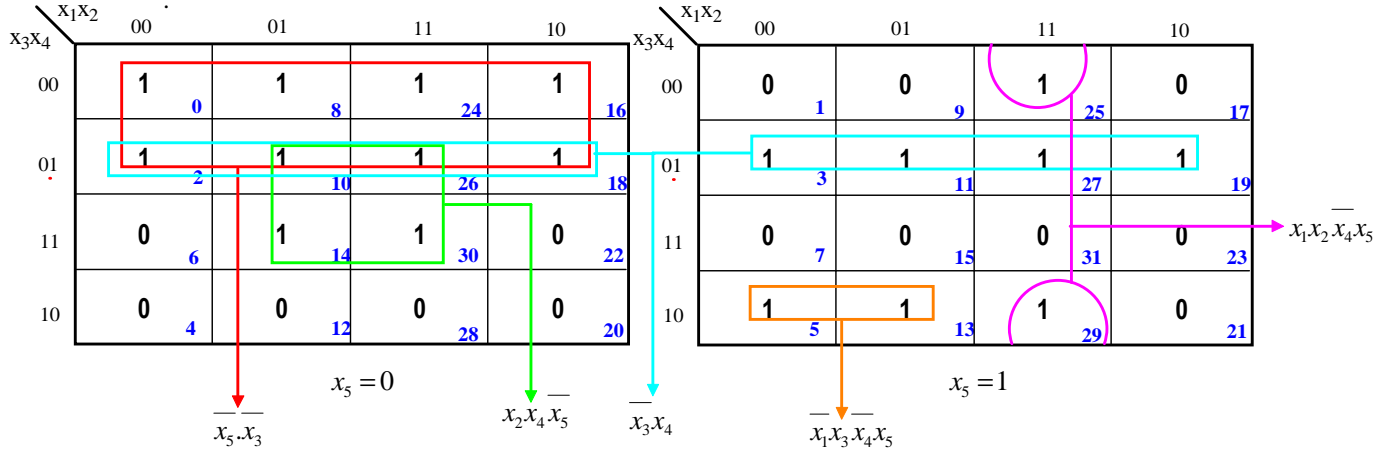4.5 Repeat problem 4.1 for the function  $f(x_1, \dots, x_5) = \prod M(1, 4, 6, 7, 9, 12, 15, 17, 20, 21, 22, 23, 28, 31)$ .


Solution:

$$f(x_1, x_2, x_3, x_4, x_5) = \prod M(1, 4, 6, 7, 9, 12, 15, 17, 20, 21, 22, 23, 28, 31)$$



or
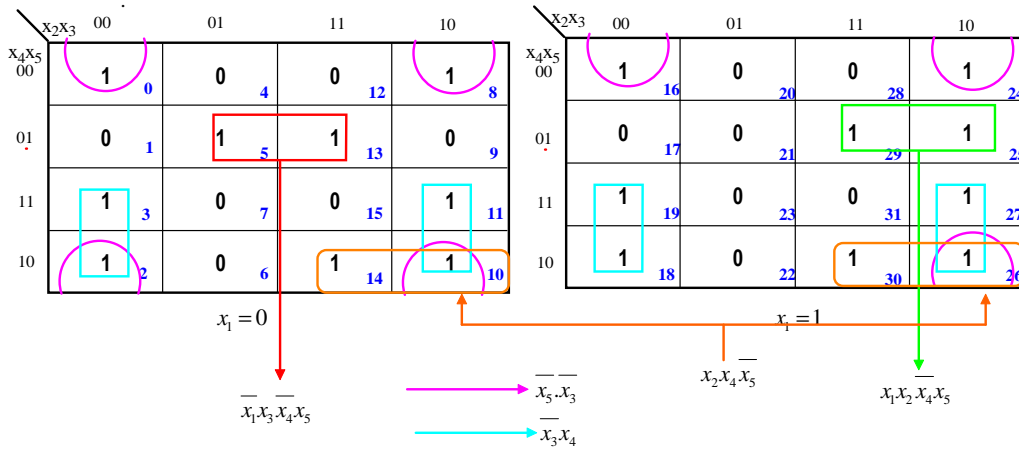
$$f(x_1, x_2, x_3, x_4, x_5) = \prod M(1, 4, 6, 7, 9, 12, 15, 17, 20, 21, 22, 23, 28, 31)$$



Mapping the 1's from the K-map as follows


$$f(x_1, x_2, x_3, x_4, x_5) = \overline{x_3} \cdot \overline{x_5} + x_2 \cdot x_4 \cdot x_5 + x_3 \cdot x_4 + \overline{x_1} \cdot \overline{x_3} \cdot x_4 \cdot x_5 + x_1 \cdot x_2 \cdot x_4 \cdot x_5$$

This is the minimum-cost SOP form.



$$f(x_1, x_2, x_3, x_4) = \sum m(7, 11, 13, 14, 15)$$

x1	x2	x3	x4	f
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

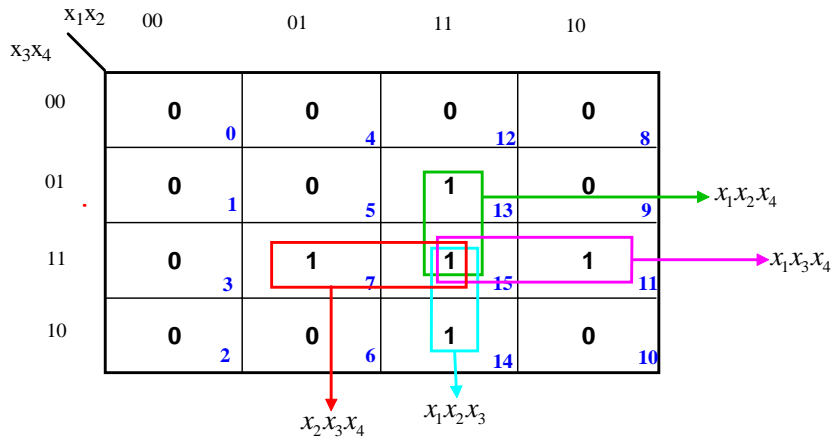

Mapping the 1's from the K-map as follows

$$f(x_1, x_2, x_3) = x_1x_2x_3 + x_1x_2x_4 + x_2x_3x_4 + x_1x_3x_4 \text{ -This is the minimum-cost SOP form.}$$

**4.12** A circuit with two outputs has to implement the following functions

$$f(x_1, \dots, x_4) = \sum m(0, 2, 4, 6, 7, 9) + D(10, 11)$$


$$g(x_1, \dots, x_4) = \sum m(2, 4, 9, 10, 15) + D(0, 13, 14)$$

Design the minimum-cost circuit and compare its cost with combined costs of two circuits that implement  $f$  and  $g$  separately. Assume that the input variables are available in both uncomplemented and complemented forms.

Solution:

The Karnaugh Map for getting the minimum cost SOP form for the function  $f$  is:
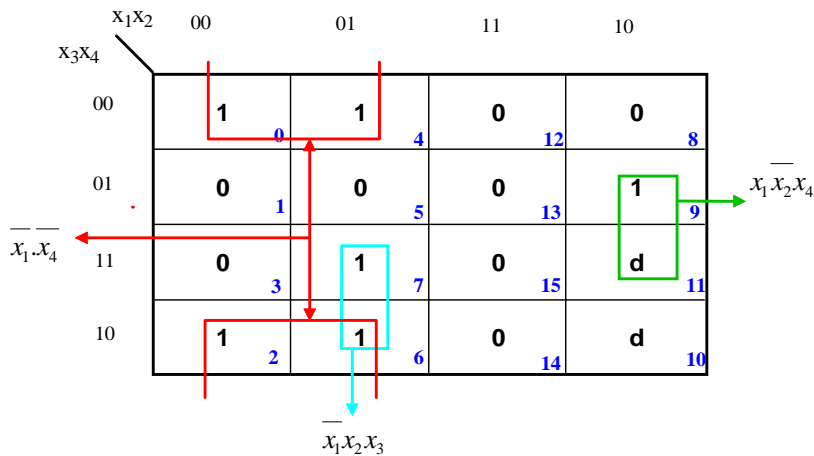
$$f(x_1, x_2, x_3, x_4) = \sum m(0, 2, 4, 6, 7, 9) + D(10, 11)$$



From the Karnaugh map the minimum cost SOP expression is

$$f(x_1, x_2, x_3, x_4) = x_1 \cdot x_4 + x_1x_2x_3 + x_1x_2x_4$$

The realization of function requires,

Two 3-input AND gate.


One 2-input AND gate.

One 3-input OR gate.

The number of gates needed to implementation the function is:

The cost of f=total no. of gates+ total no of inputs=(2+1+1)+{(2)(3)+(2)(1)+(3)(1)}=15
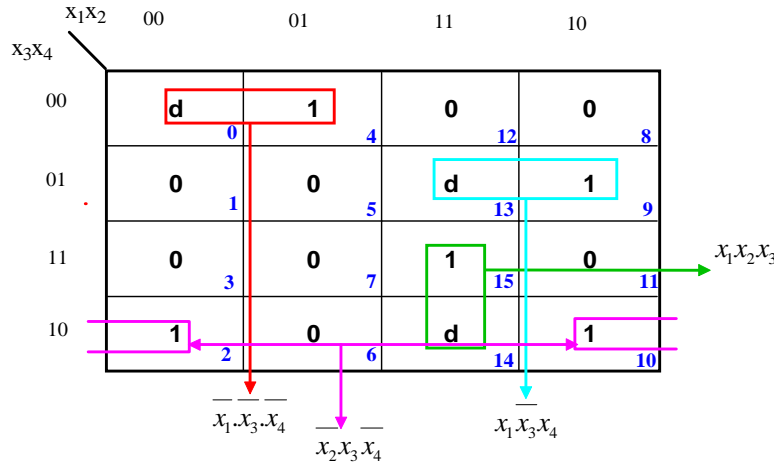
$$g(x_1, x_2, x_3, x_4) = \sum m(2, 4, 9, 10, 15) + D(0, 1, 3, 14)$$



From the Karnaugh map the minimum cost SOP expression is

$$g(x_1, x_2, x_3, x_4) = \overline{x_1} \cdot \overline{x_3} \cdot \overline{x_4} + \overline{x_2} \cdot \overline{x_3} \cdot \overline{x_4} + x_1 x_3 x_4 + x_1 x_2 x_3$$

The realization of this function requires,

Four 3-input AND gate.


One 4-input OR gate.

The number of gates needed to implementation the function is:

The cost of g=total no. of gates+ total no of inputs=(4+1)+{(3)(4)+(4)(1)}=21

The total cost of realization of function f and g is=15+21=36

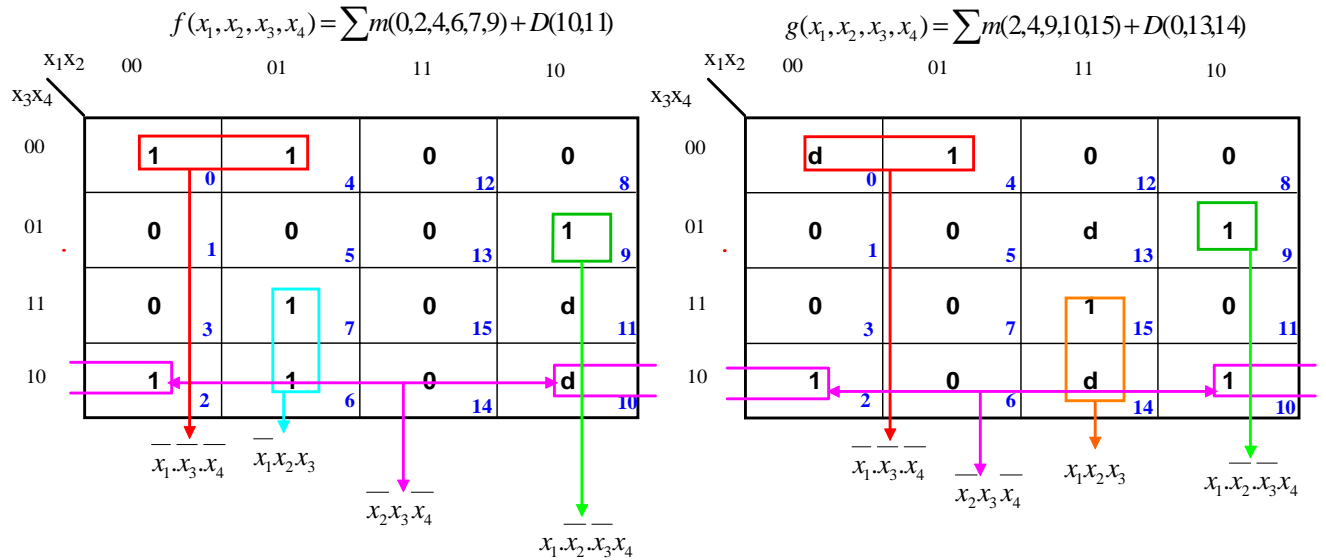In order to find the combined cost of implementing both the function f and g, we draw the Karnaugh map of f and g and grouped the elements such that both the function have as many common grouping as they possibly can have. Hence the resultant modified Karnaugh maps



Modified minimum cost SOP forms are

$$f(x_1, x_2, x_3, x_4) = \overline{x_1} \cdot \overline{x_3} \cdot \overline{x_4} + \overline{x_2} \cdot x_3 \cdot \overline{x_4} + x_1 \cdot x_2 \cdot \overline{x_3} \cdot \overline{x_4} + x_1 \cdot x_2 \cdot x_3$$

$$g(x_1, x_2, x_3, x_4) = \overline{x_1} \cdot \overline{x_3} \cdot \overline{x_4} + \overline{x_2} \cdot x_3 \cdot \overline{x_4} + x_1 \cdot x_2 \cdot \overline{x_3} \cdot \overline{x_4} + x_1 \cdot x_2 \cdot x_3$$

Hence the first three terms are shared between the two functions.

The implementation of both the functions require:

Four 3-input AND gate

One 4-input AND gate

Two 4-input OR gate

Now the combine cost of the system is

The cost of system = total no. of gates + total no. of inputs =  $(4+1+2) + \{(3)(4) + (4)(1) + (4)(2)\} = 31$

4.14 Implement the logic circuit in Figure 4.23 using NAND gates only.

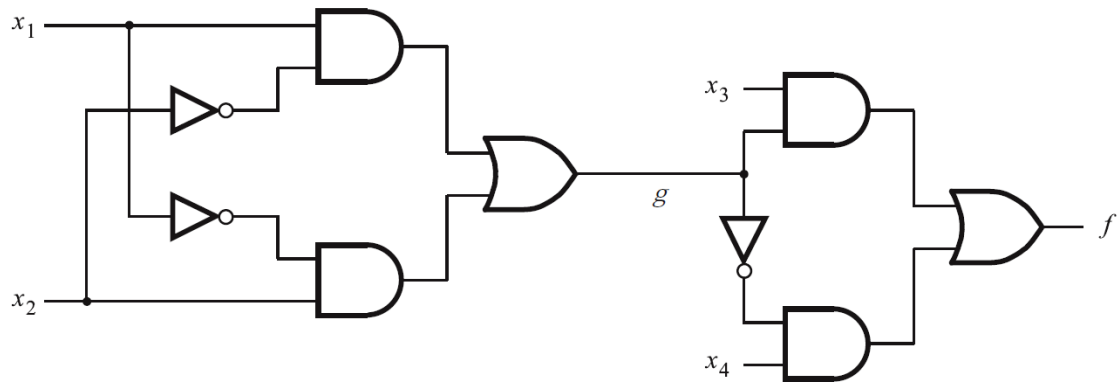


Figure 4.23 Logic circuit for Example 4.6.

Solution: the followings are the logic functions for g and f:

$$g(x_1, x_2) = x_1 \cdot \overline{x_2} + \overline{x_1} x_2$$

$$f(x_3, x_4, g) = x_3 g + \overline{g} x_4$$

Now implementing the logic using only NAND gate can be done by considering the following relationships

$$\overline{A} = \overline{(A \cdot A)} = (A \uparrow A)$$

$$A + B = \overline{\overline{A} \cdot \overline{B}} = (A \uparrow A) \uparrow (B \uparrow B)$$

$$AB = \overline{\overline{AB}} = (A \uparrow B) \uparrow (A \uparrow B)$$

Implementation of given logic function using only NAND gate is:

$$g(x_1, x_2) = x_1 \cdot \overline{x_2} + \overline{x_1} x_2 = \overline{\overline{x_1 \cdot \overline{x_2} + \overline{x_1} x_2}} = \overline{\overline{x_1 \cdot \overline{x_2}} \cdot \overline{\overline{x_1} x_2}}$$

$$\overline{x_1 \cdot \overline{x_2}} = \overline{x_1 \cdot x_2 \cdot x_2} = x_1 \uparrow (x_2 \uparrow x_2)$$

$$\overline{\overline{x_1} x_2} = \overline{x_1 \cdot x_1 \cdot x_2} = (x_1 \uparrow x_1) \uparrow x_2$$

$$g = \left[ (x_1 \uparrow (x_2 \uparrow x_2)) \right] \uparrow \left[ (x_1 \uparrow x_1) \uparrow x_2 \right]$$

$$f(x_3, x_4, g) = x_3 g + \overline{g} x_4 = \overline{\overline{x_3 g + \overline{g} x_4}} = \overline{\overline{x_3 g} \cdot \overline{\overline{g} x_4}}$$

$$\overline{\overline{x_3 g}} = x_3 \uparrow g$$

$$\overline{\overline{g} x_4} = \overline{g \uparrow x_4} = (g \uparrow g) \uparrow x_4$$

$$f = \left[ x_3 \uparrow g \right] \uparrow \left[ (g \uparrow g) \uparrow x_4 \right]$$

